



Technical Documentation

48 Output Wired and Programmable  
Pyrotechnic Ignition System  
based on the ATTINY 861

by Markus K. *alias inimodo*

2023

## Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Hardware</b>	<b>3</b>
2.1	Concept . . . . .	3
2.2	Components . . . . .	4
2.2.1	Ignition Voltage Generator . . . . .	4
2.2.1.1	The Circuit . . . . .	4
2.2.1.2	How does the circuit work? . . . . .	5
2.2.2	Controller . . . . .	6
2.2.2.1	Circuit . . . . .	6
2.2.2.2	Housing . . . . .	6
2.2.3	Trigger . . . . .	6
2.2.3.1	Circuit . . . . .	6
2.2.3.2	Housing . . . . .	6
2.2.4	Module . . . . .	6
2.2.4.1	Circuit . . . . .	6
2.2.4.2	Housing . . . . .	6
<b>3</b>	<b>Firmware</b>	<b>6</b>
3.0.1	USB Connection . . . . .	6
3.0.1.1	Program Mode . . . . .	6
3.0.1.2	Commands . . . . .	6
<b>4</b>	<b>Software</b>	<b>6</b>
<b>5</b>	<b>Recognitions</b>	<b>7</b>

## 1 Introduction

The ZK-48 (German "Zündkasten 48 Ausgänge") ignition system was developed because there are no affordable cheap programmable systems. The goal is a low cost yet reliable and robust device that works in any condition. This document provides all information surrounding this project and anyone with basic knowledge in electronics should be able to rebuild it. Although this should not be viewed as an instruction on how to build this device, but the author hopes it is useful anyway to a pyrotechnic and or electronics enthusiast. The finished device is shown in Figure 1 with the trigger on the right and one module on the left.

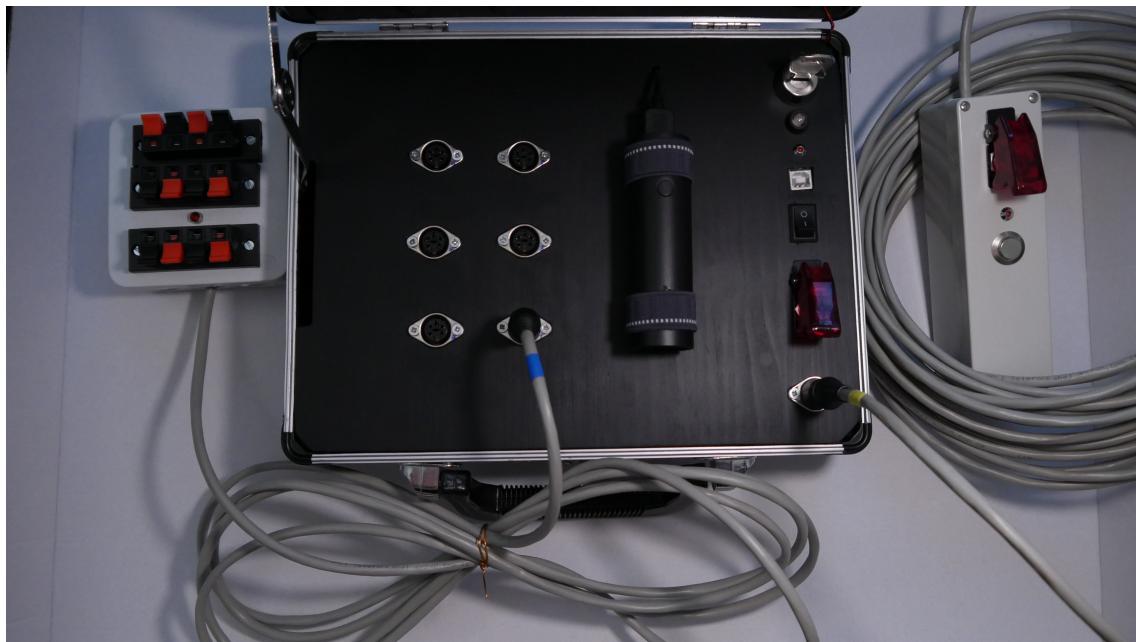


Figure 1: The resulting complete system with igniter and some modules.

## 2 Hardware

### 2.1 Concept

The device is divided into three units: controller, trigger and modules (See Figure 2). The controller is the center piece, that houses the micro controller which is a ATTINY 861<sup>1</sup> from Atmel. On board the controller are the main on/off key-switch, the arm switch,a USB port for programming, status LEDs and connectors for the trigger and modules. The trigger is connected by a 15m cable to the controller and has mounted a arm switch and the trigger button. There are six modules and each module is able to ignite eight bridge wire detonators (A-Type Only). The modules are also connected by cable to the controller. Two different cable lengths were used for the modules: 3x 4m and 3x 8m. Therefore the complete system is capable of setting of 48 detonators.

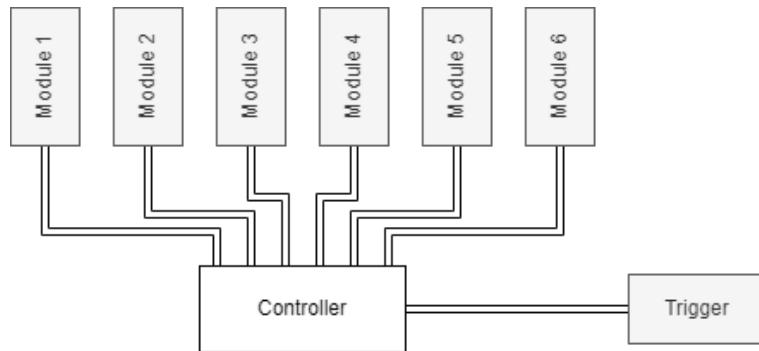


Figure 2: Basic layout of the three components controller, trigger and modules.

The system operates by the fire-and-forget principle, by which the user arms both the controller and the trigger and after pressing the trigger button the controller will automatically ignite the firework in the programmed sequence. No user input is needed after setting off. When the trigger is pressed the system goes into a 10s delay phase in order for the user to get to safety. After the delay phase is finished, the ignition phase is entered, where the programmed sequence will play through until the predetermined endpoint is reached. The trigger can be replaced with a RF-trigger although this is not recommended due safety and legal concerns in some countries. The delay period also serves as a fail safe, because if the system is triggered by accident, the user is able to abort the start by disarming the system. During the ignition phase it is also possible to halt the program by disarming the system, although re-triggering will go through the delay phase again.

The ignition sequence is programmed by USB via serial communication(See section 3.0.1). Programming the sequence can be accomplished by directly connecting to the serial port and typing the commands by hand or by using the Software provided(See section 4).

As the device is most likely placed in open-air field there is no way for it to be power by mains power, therefore it has to be powered by batteries. However, the usage of rechargeable batteries or LiPo-batteries was not desirable for this project, due cost issues and the additional requirement of protection circuits. A better alternative was found by using common 5V powerbanks for smart phones. Those already provide steady 5V with build-in protective mechanisms. Furthermore, nowadays many people use powerbanks and if the user forgets to charge or forgets the powerbank altogether, there is a high chance some will be able to provide one as replacement. A powerbank can be charged by a simple micro USB cable which is also very common and removes the need for a specialized charger.

<sup>1</sup>[https://www.mouser.com/datasheet/2/268/Atmel\\_2588\\_8\\_bit\\_AVR\\_Microcontrollers\\_tinyAVR\\_ATti-1315472.pdf](https://www.mouser.com/datasheet/2/268/Atmel_2588_8_bit_AVR_Microcontrollers_tinyAVR_ATti-1315472.pdf)

## 2.2 Components

As already explained in section 2.1, the device is split into three parts. This section will explore each part separately by looking into the design choices that were made. Although the controller is described as one unit, in reality consist of two distinct circuits. One is the ignition voltage generator (See section 2.2.1) which is responsible for generating the voltage/charge that is necessary for setting off the bridge wire detonators. The other circuit is the control logic that does the controlling (See section 2.2.2).

### 2.2.1 Ignition Voltage Generator

The step-up converter shown in Figure 3 works by the basic principle of a step-up/boost converter by storing energy in form of a magnetic field inside a inductor and releasing the energy as a current into a capacitor. Repeat this process at high frequency and a higher voltage is created at the output compared to the input voltage. For a better explanation see the document about this topic by *Texas-Instruments*<sup>2</sup>.

#### 2.2.1.1 The Circuit

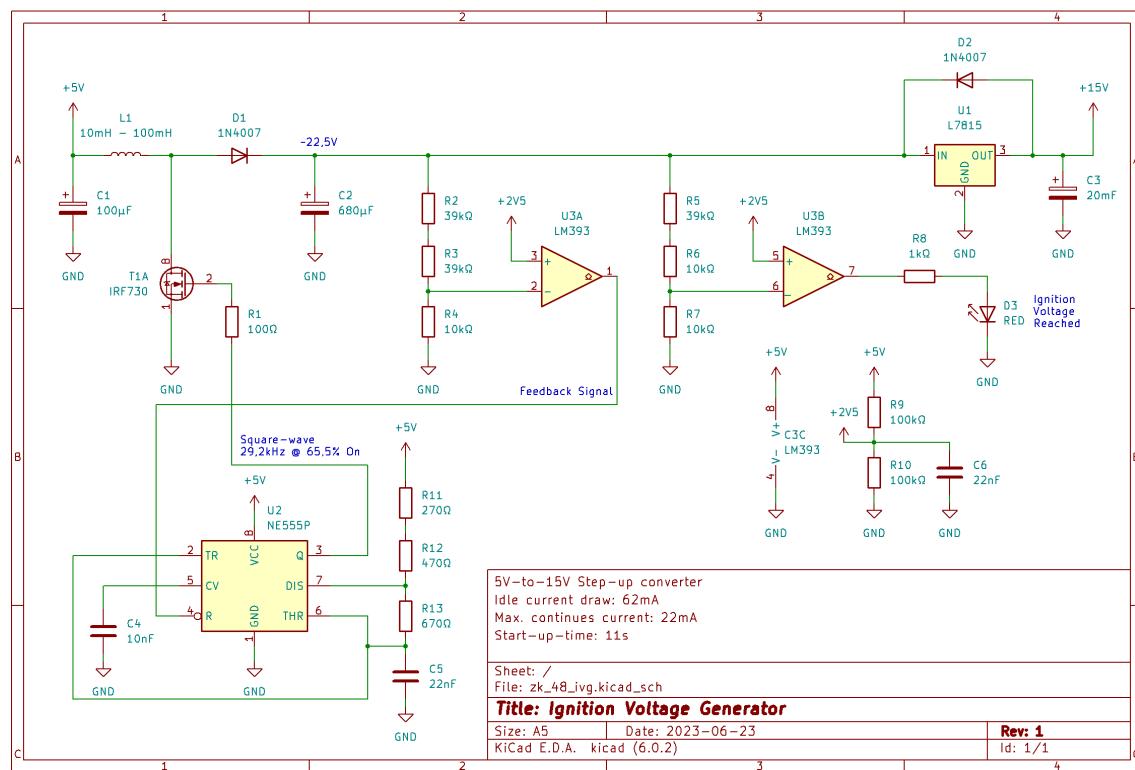


Figure 3: Circuit of the step-up converter that generates 15V DC for the ignition voltage

<sup>2</sup><https://www.ti.com/lit/an/snva731/snva731.pdf>

### 2.2.1.2 How does the circuit work?

The circuit shown in Figure 3 is made up of the popular NE555<sup>3</sup> used as oscillator, the dual comparator LM393<sup>4</sup> and a fixed linear 15V voltage regulator L7815<sup>5</sup>. The NE555 wired as a square wave oscillator generates a 29, 2kHz 5V<sub>pp</sub> signal with a 65,5% on-time. This signal is used to drive the IRF730<sup>6</sup> N-channel MOSFET which switches the current through the inductor  $L_1$  and therefore charges the capacitor  $C_2$ . We shall name this voltage the intermediate voltage.

Through a voltage divider the voltage at  $C_2$  is stepped down by a factor of  $\frac{1}{9}$  and compared to a 2,5V reference voltage by  $U_{3A}$ . This results in a 5V output signal at  $U_{3A}$  if the capacitor  $C_2$  voltage is lower than 22,5V. This signal is called the feedback signal with turns off the NE555 if the intermediate voltage has reached 22,5V. A schmitt-trigger was intentionally not used, because this would result in a oscillating turning off and on of the feedback signal which is undesirable in this configuration.

The intermediate voltage is then converted by the L7815 to stable 15V which charges the large 20mF ignition capacitor  $C_3$ . This voltage is called the ignition voltage. Equation (1) calculates the energy stored in the complete system with all six modules connected (Thus the total capacitance is 26mF, but read more in Section 2.2.4) which equates to around 3J and therefore does not present any harm or danger to life<sup>7</sup>. Touching fully charged capacitors with sweaty hands did not result in any shock or pain.

$$W_{el} = \frac{U^2 \cdot C_{tot}}{2} = \frac{(15V)^2 \cdot 26mF}{2} = 2,925J \quad (1)$$

The second comparator  $U_{3B}$  in the LM393 package was used to turn on a red LED  $D_3$  whose purpose is to indicate whether the intermediate voltage is bigger than 14,75V. This shows the user if the system is ready for operation and if a ignition voltage is present.

*Note: Please note that the ignition voltage generator was designed by the author and is by no means ideal nor optimized. This was the first attempt at creating a step-up convert from scratch with components that were on hand. It does the job well but any bought step-up convert will do just fine and most likely better.*

---

<sup>3</sup><https://www.ti.com/lit/ds/symlink/ne555.pdf>

<sup>4</sup><https://www.ti.com/lit/ds/symlink/lm393.pdf>

<sup>5</sup><https://www.st.com/resource/en/datasheet/178.pdf>

<sup>6</sup><https://www.vishay.com/docs/91047/91047.pdf>

<sup>7</sup>[https://www.ehss.vt.edu/programs/ELR\\_capacitors.php](https://www.ehss.vt.edu/programs/ELR_capacitors.php)

## 2.2.2 Controller

### 2.2.2.1 Circuit

### 2.2.2.2 Housing

### 2.2.3 Trigger

#### 2.2.3.1 Circuit

#### 2.2.3.2 Housing

### 2.2.4 Module

#### 2.2.4.1 Circuit

#### 2.2.4.2 Housing

## 3 Firmware

### 3.0.1 USB Connection

#### 3.0.1.1 Program Mode

#### 3.0.1.2 Commands

## 4 Software

## 5 Recognitions

All circuits were drawn with the help of *KiCad* 6.0<sup>8</sup>

All flowcharts and diagrams were drawn with the help of *Drawio*<sup>9</sup>

---

<sup>8</sup><https://www.kicad.org/>  
<sup>9</sup><https://app.diagrams.net/>